

9.Design and implement 2-bit half adder using logisim simulator.

AIM: To design and implement the two bit half adder using Logisim simulator.

TRUTH TABLE:-

The half-adder is a digital circuit that adds 2 bits (A and B) generating 2 bits at the output for the sum (S) and carry (C). Its truth table is shown in below table.

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = A \text{ XOR } B \quad C = A \text{ AND } B$$

THE FOLLOWING STEPS IS USED TO DRAW A HALF-ADDER CIRCUIT.

⇒ Insert 2 inputs into the canvas. o Label the inputs (A & B) by setting the attribute 'Label' in the attribute table.

Note that both inputs have now 0s inside their green spots. These are the current bit value of the input.

⇒ Insert one XOR gate and one AND gate into the canvas.

→ The two gates are located inside the 'Gates' library in the explorer pane.

→ Change the 'Number of Inputs' in the attribute table to 2.

⇒ Insert 2 outputs in the canvas

Label the outputs (S & C).

Note that both outputs have X inside the dots.


⇒ X indicates an invalid value for the output.

Connect the inputs to the XOR gate.

Connect the inputs to the AND gate.

⇒ Start the connection on the AND gate input and finish it on the wire reaching the designated input.

Connect the outputs to the gates.

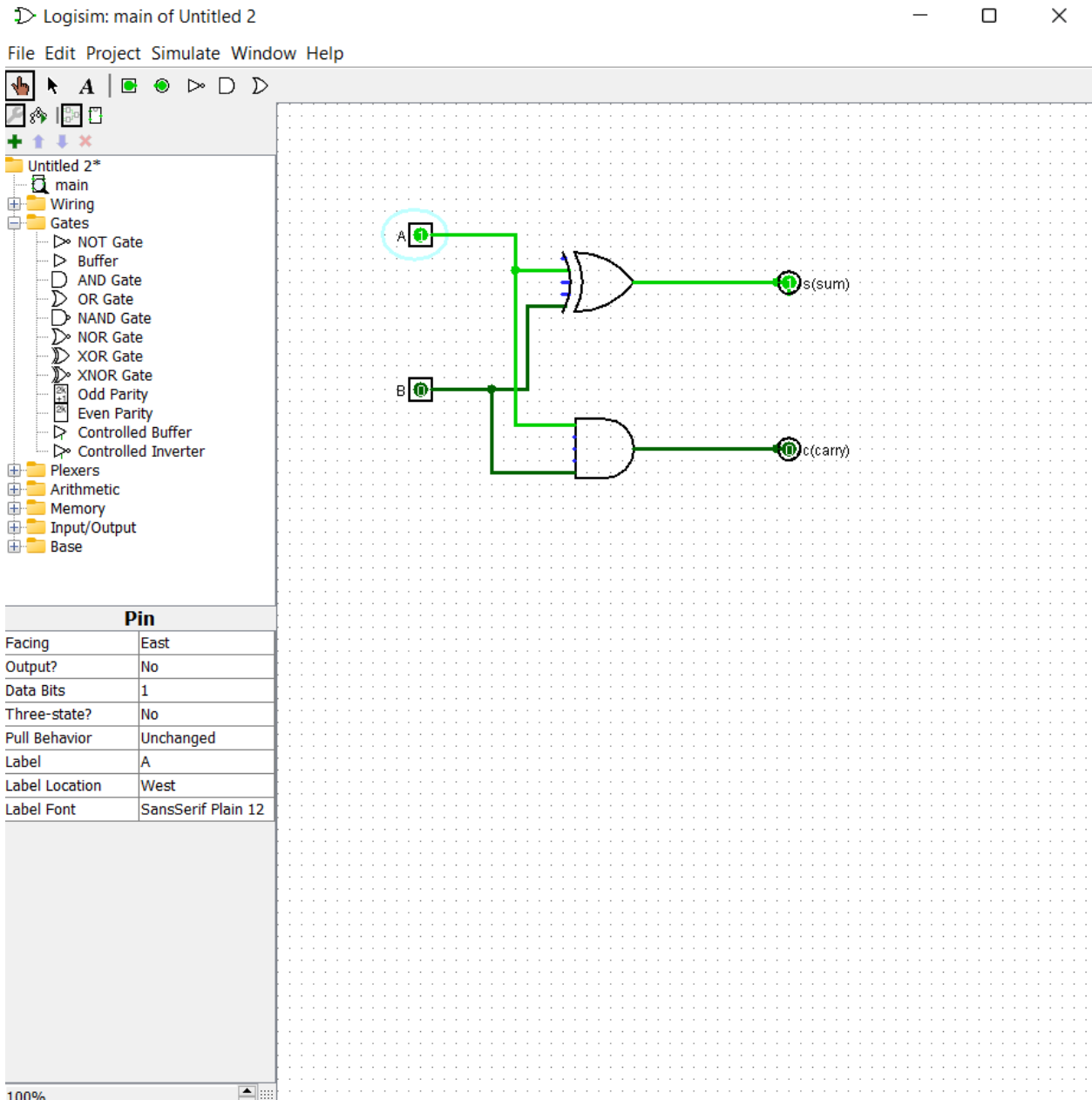

RESULT:-

Hence the designing of the 2-bit half adder using logisim simulator has been implemented successfully.